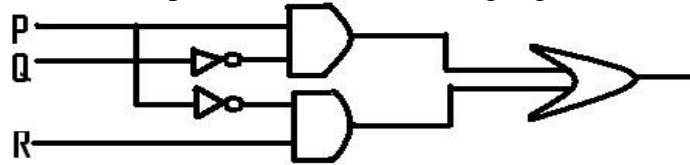


## HOLIDAYS HOMEWORK

1. (a) State and verify absorption law using truth table.  
 (b) Write the equivalent Boolean Expression for the following logic circuit:



- (c) Write the POS form of a Boolean function G, which is represented in a truth table as follows

U	V	W	G
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

- (d) Reduce the following Boolean expression using K-map:  
 $H(U,V,W,Z) = \sum(0,1,4,5,6,7,11,12,13,14,15)$


2. (a) State and Verify Absorption law in Boolean Algebra.  
 (b) Draw a logical circuit diagram for the following Boolean Expression:  $A.(B+C')$   
 (c) Convert the following Boolean expression into its equivalent Canonical Product of sum form (POS):  $A.B'C + A'.B.C + A'.B.C'$ .  
 (d) Reduce the following Boolean expression using K-map:

$$F(A,B,C,D) = \sum(0,1,2,4,5,8,9,10,11)$$

3. (a) State and verify De Morgan's law in Boolean Algebra.  
 (b) Draw a Logical Circuit Diagram for the following Boolean Expression.  $X'.(Y'+Z)$   
 (c) Convert the following Boolean expression into its equivalent Canonical Sum of Product Form (SOP):  $(X'+Y+Z').(X'+Y+Z).(X'+Y'+Z).(X'+Y'+Z')$   
 (d) Reduce the following Boolean Expression using K-map.


$$F(A,B,C,D) = \sum(0,2,3,4,6,7,8,10,12)$$

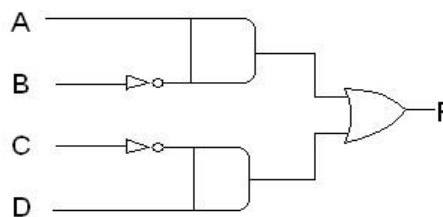4. (a) State De Morgan's Theorems and verify the same using truth table.  
 (b) Write the equivalent canonical product of sum expression for the following sum of product expression:  $F(X, Y,Z) = \sum(0, 2,4,5)$   
 (c) Write the equivalent Boolean expression for the following logic circuit



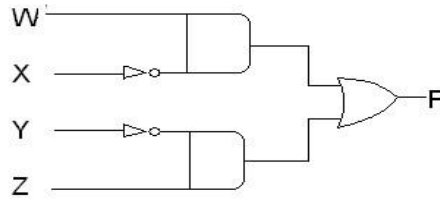
- (d) Reduce the following Boolean expression using K - Map :  
 $F(A, B, C, D,) = \Pi(5, 6, 7, 8, 9, 12, 13, 14, 15)$

- 5 (a) State Distributive law and verify the same using truth table.  
 (b) Write the equivalent Boolean expression for the following logic circuit




- (c) Reduce the following Boolean expression using K – Map :  
 $F(U, V, W, Z) = \sum(0,1,2,3,4,10,11)$

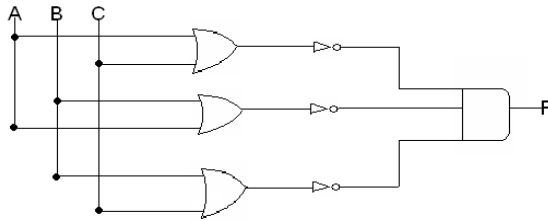6. (a) State and verify Associative Law.  
 (b) Write the equivalent expression for the following Logic Circuit :




- (c) Express  $P + Q'R$  in POS form.  
 (d) Reduce the following Boolean expression using K – Map :  
 $F(P, Q, R, S) = \Pi(0,3,5,6,7,11,12,15)$

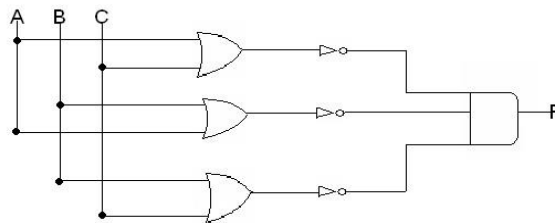7. (a) State and verify Distributive Law algebraically.  
 (b) Write the equivalent expression for the following Logic Circuit :



- (c) Reduce the following Boolean expression using K – Map :  
 $F(P, Q, R, S) = \sum(0,3,5,6,7,11,12,15)$

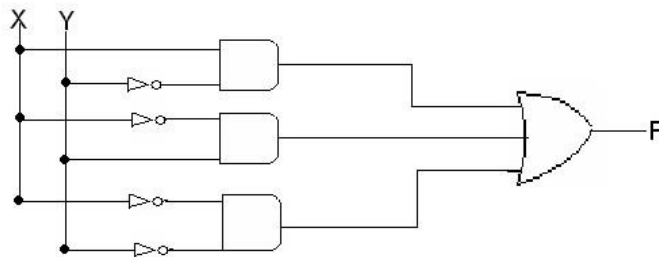8. (a) Write the equivalent expression for the following Logic Circuit :




(b) Write the POS form of a Boolean Function F, Which is represented by the following truth table:

X	Y	Z	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

(c) Reduce the following Boolean expression using K – Map :

$$F(A, B, C, D,) = \sum(0,1,2,3,4,5,10,11,15)$$

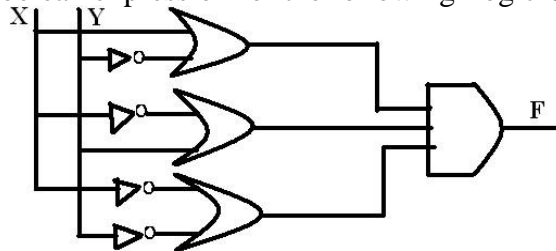9. (a) Write the equivalent Boolean expression for the following Logic Circuit:



(b) Write the SOP form of a Boolean Function F, Which is represented by the following truth table:

A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

(c) Reduce the following Boolean expression using K – Map :

$$F(A, B, C, D,) = \Pi (0,1,2,3,4,5,10,11,15)$$

10 (a) Give the following truth table, derive a sum of product (SOP) and Product of Sum (POS) Form of Boolean expression from it:

A	B	C	F(A,B,C)
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

(b) Obtain a simplified form for the following Boolean Expression using Karnaugh Map:


$$F(a,b,c,d) = \sum(0,1,2,4,5,7,8,9,10,11,14)$$

11. (a) State De Morgan's Laws. Verify one of the De Morgan's Laws using a truth table.  
 (b) Verify  $X.Y'Z+X.Y'Z'+X'.Y'Z = X.Y' + Y'.Z$  algebraically.  
 (c) Write the dual of the Boolean Expression:  
 $(B'+C).A$   
 (d) Obtain a simplified form for a Boolean Expression:  
 $F(U,V,W,Z) = \sum(0,2,3,4,7,9,10,13,14,15)$

12. (a) Prove  $XY + YZ + Y'Z = XY + Z$ , algebraically.  
 (b) Obtain the simplified form, of a Boolean expression using Karnaugh map.  
 $F(w,x,y,z) = \sum(2,3,6,10,11,14)$   
 (c) Represent the Boolean expression  $(X+Y)(Y+Z)(X+Z)$  with help of NOR gates only.  
 (d) Given the following truth table, write the product of sums form of the function.

X	Y	Z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

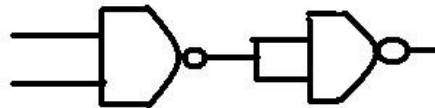13. (a) State and verify Duality Principle.  
 (b) Prove algebraically:  $x'y'z' + x'y'z + x'yz' + x.y'z = x' + y'$   
 (c) If  $F(a,b,c,d) = \Pi(0,1,3,4,5,7,8,9,11,12,13,15)$ , Obtain the simplified form using K-map.  
 (d) Seven inverters are cascaded one after another. What is the output if the input is 1?  
 (e) Given the following circuit:



What is the output if (i) both inputs are FALSE(0) (ii) one is FALSE and the other is TRUE.

14. (a) Prove  $X'.Y+Y'.Z=X'.Y.Z+X'.Y'.Z'+X.Y'.Z+X'.Y'.Z$  algebraically.  
 (b) Obtain simplified form for a boolean expression  
 $F(x,y,z,w) = \sum(1,3,4,5,7,9,11,12,13,15)$  using Karnaugh Map.  
 (d) Represent the Boolean expression  $X'Y+Y'Z$  with the help of NAND gates only.  
 (e) Write the Sum of Products form of the function  $G(U,V,W)$ . Truth table representation of G is as follows:

U	V	W	G
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

15. (a) Prove  $x+x'y=x+y$  algebraically.  
 (b) Write the dual of the Boolean expression  $(x+y).(x'+y')$   
 (c) Minimise  $F(w,x,y,z)$  using Karnaugh map.  
 $F(w,x,y,z) = \sum (0,4,8,12)$   
 (d) Represent the Boolean expression  $(x+y)(y+z)(z+x)$  with the help of NOR gates only.  
 (e) Write sum of product form of the function  $F(x,y,z)$ . The truth table representation for the function  $F$  is given below:

X	Y	Z	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

**ALL THE BEST**